

Chapter 27 Circuits

02. The chemical energy of the battery is reduced by $\Delta E = q\varepsilon$, where q is the charge that passes through in time $\Delta t = 6.0$ min, and ε is the emf of the battery. If i is the current, then $q = i\Delta t$ and

$$E = I\varepsilon\Delta t = (5.0\text{ A})(6.0\text{ V})(6.0\text{ min})(60\text{ s/min}) = 1.1 \times 10^4\text{ J}.$$

03. If P is the rate at which the battery delivers energy and Δt is the time, then $\Delta E = P\Delta t$ is the energy delivered in time Δt . If q is the charge that passes through the battery in time Δt and ε is the emf of the battery, then $\Delta E = q\varepsilon$. Equating the two expressions for ΔE and solving for Δt , we obtain

$$\Delta t = \frac{q\varepsilon}{P} = \frac{(120\text{ Ah})(12.0\text{ V})}{100\text{ W}} = 14.4\text{ h}.$$

06. The current in the circuit is

$$i = (150\text{ V} - 50\text{ V}) / (3.0\ \Omega + 2.0\ \Omega) = 20\text{ A}.$$

So from $V_Q + 150\text{ V} - (2.0\ \Omega)i = V_P$, we get $V_Q = 100\text{ V} + (2.0\ \Omega)(20\text{ A}) - 150\text{ V} = -10\text{ V}$.

18. (a) $R_{eq}(FH) = (10.0)(10.0)(5.00) / [(10.0)(10.0) + 2(10.0)(5.00)] = 2.50\ (\Omega)$. (b) $R_{eq}(FG) = (5.00)\text{ R} / (R + 5.00)$, where $R = 5.00 + (5.00)(10.0) / (5.00 + 10.0) = 8.33\ (\Omega)$. So $R_{eq}(FG) = (5.00)(8.33) / (5.00 + 8.33) = 3.13\ (\Omega)$.

23. First, we note V_4 , that the voltage across R_4 is equal to the sum of the voltages across R_5 and R_6 :

$$V_4 = i_6(R_5 + R_6) = (1.40)(8.00 + 4.00) = 16.8\text{ (V)}.$$

The current through R_4 is then equal to $i_4 = V_4/R_4 = 16.8/16.0 = 1.05\text{ (A)}$. By the junction rule, the current in R_2 is $i_2 = i_4 + i_6 = 1.05 + 1.40 = 2.45\text{ (A)}$, so its voltage is $V_2 = (2.00)(2.45) = 4.90\text{ (V)}$. The loop rule tells us the voltage across R_3 is $V_3 = V_2 + V_4 = 21.7\text{ V}$ (implying that the current through it is $i_3 = V_3/2.00 = 10.85\text{ A}$). The junction rule now gives the current in R_1 as $i_1 = i_2 + i_3 = 2.45 + 10.85 = 13.3\text{ (A)}$, implying that the voltage across it is $V_1 = (13.3)(2.00) = 26.6\text{ (V)}$. Therefore, by the loop rule, $\varepsilon = V_1 + V_3 = 26.6 + 21.7 = 48.3\text{ (V)}$.

27. (a) We note that the R_1 resistors occur in series pairs, contributing net resistance $2R_1$ in each branch where they appear. Since $\varepsilon_2 = \varepsilon_3$ and $R_2 = 2R_1$, from symmetry we know that the currents through ε_2 and ε_3 are the same: $i_2 = i_3 = i$. Therefore, the current through ε_1 is $i_1 = 2i$. Then from $V_b - V_a = \varepsilon_2 - iR_2 = \varepsilon_1 + (2R_1)(2i)$ we obtain

$$i = \frac{\varepsilon_2 - \varepsilon_1}{4R_1 + R_2} = \frac{4.0 - 2.0}{4(1.0) + 2.0} = 0.33\text{ (A)}.$$

Therefore, the current through ε_1 is $i_1 = 2i = 0.67\text{ A}$. (b) The direction of i_1 is downward. (c) The current through ε_2 is $i_2 = 0.33\text{ A}$. (d) The direction of i_2 is upward. (e) From part (a), we have $i_3 = i_2 = 0.33\text{ A}$. (f) The direction of i_3 is also upward. (g) $V_a - V_b$

$$= -iR_2 + \varepsilon_2 = -(0.333)(2.0) + 4.0 = 3.3\text{ (V)}.$$

33. (a) We first find the currents. Let i_1 be the current in R_1 and take it to be positive if it is to the right. Let i_2 be the current in R_2 and take it to be positive if it is to the left. Let i_3 be the current in R_3 and take it to be positive if it is upward. The junction rule produces

$$i_1 + i_2 + i_3 = 0.$$

The loop rule applied to the left-hand loop produces

$$\varepsilon_1 - i_1 R_1 + i_3 R_3 = 0,$$

and applied to the right-hand loop produces

$$\varepsilon_2 - i_2 R_2 + i_3 R_3 = 0.$$

We substitute $i_3 = -i_2 - i_1$, from the first eq., into the other two to obtain

$$\varepsilon_1 - i_1 R_1 - i_2 R_2 - i_3 R_3 = 0$$

and $\varepsilon_2 - i_2 R_2 - i_2 R_3 - i_1 R_3 = 0.$

Solving the above equations yield

$$i_1 = \frac{\varepsilon_1(R_2 + R_3) - \varepsilon_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} = 0.421\text{ (A)}$$

$$= \frac{(3.00)(2.00 + 5.00) - (1.00)(5.00)}{(4.00)(2.00) + (4.00)(5.00) + (2.00)(5.00)}$$

$$i_2 = \frac{\varepsilon_2(R_1 + R_3) - \varepsilon_1 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} = -0.158\text{ (A)}$$

$$= \frac{(1.00)(4.00 + 5.00) - (3.00)(5.00)}{(4.00)(2.00) + (4.00)(5.00) + (2.00)(5.00)}$$

$$i_3 = -\frac{\varepsilon_2 R_1 + \varepsilon_1 R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} = -0.263\text{ (A)}$$



$$= -\frac{(1.00)(4.00) + (3.00)(2.00)}{(4.00)(2.00) + (4.00)(5.00) + (2.00)(5.00)}$$

Note that the current i_3 in R_3 is actually downward and the current i_2 in R_2 is to the right. The current i_1 in R_1 is to the right. (a) The power dissipated in R_1 is $P_1 = i_1^2 R_1 = (0.421)^2(4.00) = 0.709\text{ (W)}$. (b) The power dissipated in R_2 is $P_2 = i_2^2 R_2 = (-0.158)^2(2.00) = 0.0499 \approx 0.050\text{ (W)}$. (c) The power dissipated in R_3 is $P_3 = i_3^2 R_3 = (-0.263)^2(5.00) = 0.346\text{ (W)}$. (d) The power supplied by ε_1 is $i_3 \varepsilon_1 = (0.421)(3.00) = 1.26\text{ (W)}$. (e) The power “supplied” by ε_2 is $i_2 \varepsilon_2 = (-0.158)(1.00) = -0.158\text{ (W)}$. The negative sign indicates that ε_2 is actually absorbing energy from the circuit.

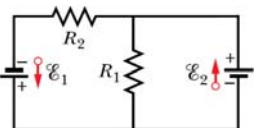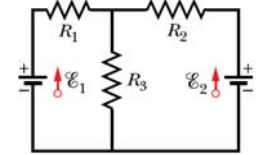66. (a) The loop rule (proceeding counterclockwise around the right loop) leads to $\varepsilon_2 - i_1 R_1 = 0$ (where i_1 was assumed downward). This yields $i_1 = 0.0600\text{ A}$. (b) The direction of i_1 is downward. (c) The loop rule (counterclockwise around the left loop) gives

$$(+\varepsilon_1) + (+i_1 R_1) + (-i_2 R_2) = 0,$$


where i_2 has been assumed leftward. This yields $i_3 = 0.180\text{ A}$. (d) A positive value of i_3 implies that our assumption on the direction is



correct, i.e., it flows leftward. (e) The junction rule tells us that the current through the 12 V battery is $0.180 + 0.0600 = 0.240$ (A). (f) The direction is upward.

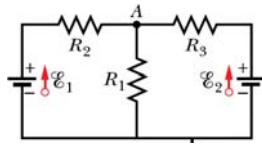95. (a) Using the junction rule ($i_1 = i_2 + i_3$) we write two loop rule equations:

$$\begin{aligned} \varepsilon_1 - i_2 R_2 - (i_2 + i_3) R_1 &= 0, \\ \varepsilon_2 - i_3 R_3 - (i_2 + i_3) R_1 &= 0. \end{aligned}$$



Solving, we find $i_2 = 0.0109$ A (rightward, as was assumed in writing the equations as we did), $i_3 = 0.0273$ A (leftward), and $i_1 = i_2 + i_3 = 0.0382$ A (downward). (b) downward. See the results in part (a). (c) $i_2 = 0.0109$ A. See the results in part (a). (d) rightward. See the results in part (a). (e) $i_3 = 0.0273$ A. See the results in part (a). (f) leftward. See the results in part (a). (g) The voltage across R_1 equals $V_A: (0.0382 \text{ A})(100 \Omega) = +3.82 \text{ V}$.

45. During charging, the charge on the positive plate of the capacitor is given by $q = C\varepsilon(1 - e^{-t/\tau})$, where C is the capacitance, ε is applied emf, and $\tau = RC$ is the capacitive time constant. The equilibrium charge is $q_{\text{eq}} = C\varepsilon$. We require $q = 0.99q_{\text{eq}} = 0.99C\varepsilon$, so $0.99 = 1 - e^{-t/\tau}$. Thus, $e^{-t/\tau} = 0.01$. Taking the natural logarithm of both sides, we obtain $t/\tau = -\ln 0.01 = 4.61$ or $t = 4.61\tau$.

46. (a) $\tau = RC = (1.40 \times 10^6)(1.80 \times 10^{-6}) = 2.52$ (s). (b) $q_0 = \varepsilon C = (12.0)(1.80 \mu) = 21.6 \mu\text{C}$. (c) The time t satisfies $q = q_0(1 - e^{-t/RC})$, or

$$t = RC \ln \frac{q_0}{q_0 - q} = (2.52) \ln \frac{21.6}{21.6 - 16.0} = 3.40 \text{ (s)}.$$

48. Here we denote the battery emf as V . Then the requirement stated in the *Pb* that the resistor voltage be equal to the capacitor voltage becomes $iR = V_C$, or $Ve^{-t/RC} = V(1 - e^{-t/RC})$, where Eqs. 27-34 and 35 have been used. This leads to $t = RC \ln 2$, or $t = 0.208$ ms.

53. At $t = 0$ the capacitor is completely uncharged and the current in the capacitor branch is as it would be if the capacitor were replaced by a wire. Let i_1 be the current in R_1 and take it to be positive if it is to the right. Let i_2 be the current in R_2 and take it to be positive if it is downward. Let i_3 be the current in R_3 and take it to be positive if it is downward. The junction rule produces $i_1 = i_2 + i_3$ the loop rule applied to the left-hand loop produces $\varepsilon_1 - i_1 R_1 + i_2 R_2 = 0$, and the loop rule applied to the right-hand loop produces $i_2 R_2 - i_3 R_3 = 0$.

Since the resistances are all the same we can simplify the mathematics by replacing R_1 , R_2 , and R_3 with R . (a) Solving the three simultaneous eqs., we find $i_1 = 2\varepsilon/3R = 2(1.2 \times 10^3)/[3(0.73 \times 10^6)] = 1.1 \times 10^{-3}$ A. (b) $i_2 = \varepsilon/3R = (1.2 \times 10^3)/[3(0.73 \times 10^6)] =$

5.5×10^{-4} A. (c) $i_3 = i_2 = 5.5 \times 10^{-4}$ A. At $t = \infty$ the capacitor is fully charged and the current in the capacitor branch is 0. Thus, $i_1 = i_2$, and the loop rule yields $\varepsilon_1 - i_1 R_1 + i_1 R_2 = 0$. (d) The solution is $i_1 = \varepsilon/2R = (1.2 \times 10^3)/[2(0.73 \times 10^6)] = 8.2 \times 10^{-4}$ A. (e) $i_2 = i_1 = 8.2 \times 10^{-4}$ A. (f) As stated before, the current in the capacitor branch is $i_3 = 0$. We take the upper plate of the capacitor to be positive. This is consistent with current flowing into that plate. The junction equation is $i_1 = i_2 + i_3$, and the loop equations are

$$\varepsilon - i_1 R - i_2 R = 0 \quad \text{and} \quad -(q/C) - i_3 R + i_2 R = 0.$$

We use the first eq. to substitute for i_1 in the second and obtain $\varepsilon - 2i_2 R - i_3 R = 0$. Thus $i_2 = (\varepsilon - i_3 R)/2R$. We substitute this expression into the third eq. above to obtain $-(q/C) - (i_3 R) + (\varepsilon/2) - (i_3 R/2) = 0$. Now we replace i_3 with dq/dt to obtain

$$\frac{3R}{2} \frac{dq}{dt} + \frac{q}{C} = \frac{\varepsilon}{2}.$$

This is just like the eq. for an RC series circuit, except that the time constant is $\tau = 3RC/2$ and the impressed potential difference is $\varepsilon/2$. The solution is

$$q = \frac{1}{2} C\varepsilon (1 - e^{-2t/3RC}).$$

The current in the capacitor branch is

$$i_3(t) = \frac{dq}{dt} = \frac{\varepsilon}{3R} e^{-2t/3RC}.$$


The current in the center branch is

$$i_2(t) = \frac{\varepsilon}{2R} - \frac{1}{2} i_3 = \frac{\varepsilon}{2R} - \frac{\varepsilon}{6R} e^{-2t/3RC} = \frac{\varepsilon}{6R} (3 - e^{-2t/3RC}).$$

and the potential difference across R_2 is

$$V_2(t) = i_2 R = \frac{1}{6} \varepsilon (3 - e^{-2t/3RC}).$$

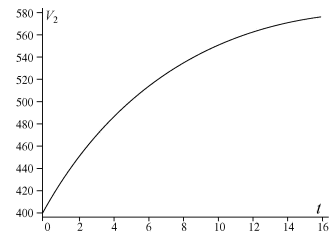(g) For $t = 0$, $e^{-2t/3RC}$ is 1 and $V_2 = \varepsilon/3 = 1.2 \times 10^3/3 = 4.0 \times 10^2$ (V). (h) For $t = \infty$, $e^{-2t/3RC} = 0$ and $V_2 = \varepsilon/2 = (1.2 \times 10^3 \text{ V})/2 = 6.0 \times 10^2$ V. (i) A plot of V_2 as a function of time is shown in the following graph.



54. In the steady state situation, the capacitor voltage will equal the voltage across $R_2 = 15 \text{ k}\Omega$:

$$V_0 = R_2 \frac{\varepsilon}{R_1 + R_2} = (15.0) \frac{20.0}{10.0 + 15.0} = 12.0 \text{ (V)}.$$

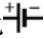
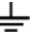

Now, multiplying Eq. 27-39 by the capacitance leads to $V = V_0 e^{-t/RC}$ describing the voltage across the capacitor (and across $R_2 = 15.0 \text{ k}\Omega$) after the switch is opened (at $t = 0$). Thus, with $t = 0.00400$ s, we obtain

$$V = (12) \exp[-0.004/(15.0 \text{ k} \times 0.400 \mu)] = 6.16 \text{ (V)}.$$

Therefore, using Ohm's law, the current through R_2 is $6.16/15000 = 4.11 \times 10^{-4}$ (A).

(如發現錯誤煩請告知, jyang@mail.ntou.edu.tw, Thanks.)

重點整理—第 27 章 直流電路

電動勢源(電源)—可對電荷載子作功並維持一定端電位差之元件；**電動勢(emf, 單位: V)** $\varepsilon = dW/dq$ 對單位正電荷由低電位端移至高位端所作的功，電路符號。**理想電動勢源**其內部無耗能機制，可提供端電位差 ε ；而**真實電動勢源**可視為一理想電動勢源 ε “串聯”一內電阻 r ，其提供端電位差 $\varepsilon - iR$ 。**迴路**：一封閉的導電路徑(自由電荷可作循環運動)。**接地**：透過導體與地面相接，電路符號，此為零電位。電阻器電路符號。

Kirchhoff's Junction Rule (Current Law)

流入或流出任一節點的電流之代數和須為零；流入任一節點的電流和須等於流出該節點的電流。
<電荷守恆 charge conservation>

Kirchhoff's Loop Rule (Voltage Law)

繞著一電路之任一迴路走一圈，所遇到的電位改變量之代數和須為零。<能量守恆>

解電路問題技巧：1.劃出電路；2.對電路之各分路，給予一電流(符號及方向)；3.運用串聯及並聯方法，減少分路；4.利用節點規則以減少電流變數；5.利用迴路規則解出各電流變數。

SI. 鎳氫或鋰類可充電電池以 mAh (毫安培小時)表示儲存電荷量，1 mAh = 3.6 C。**S2. 用電安全**：最重要守則—勿使身體接觸高低電位而使電流通過身體或過電流使用；用電不當，造成觸電，可能致命，或電路走火引起生命財產的損失！**電擊之危險**：(1)引起心臟或肺部發生問題，(2)致命的燒傷。**家居電線**：傳統的為二線改用三線(含接地線)最安全：其為火(平)/中性(平)/接地(圓)線，或者使用較安全二線“極性插頭”[寬(中性)口及窄(火)口]。

電位差(電壓)符號規則：一般規則—電位減少(增加)， $-(+)V$ ；**a. 順(逆)著電流通過電阻器**， $-(+)iR$ ；**b. 從電容器正(負)板移動到負(正)板**， $-(+)q/C$ ；**c. 從電源正(負)端移動到負(正)端**， $-(+)\varepsilon$ 。

電阻器串聯：**a. 流經各電阻器之電流皆相等**，**b. 總電位差等於各電阻器之電位差和** $V_{ab} = \sum_i V_i$ ，**c. 等效電阻** $R_{eq} = \sum_i R_i$ ， $R_{eq} > R_i$ 。

電阻器並聯：**a. 各電阻器兩端之電位差皆相等**，**b. 總電流等於經各電阻器之電流和** $I = \sum_i I_i$ ，**c. 等效電阻** $R_{eq}^{-1} = \sum_i R_i^{-1}$ ， $R_{eq} < R_i$ 。

RC 電路—電阻器 R 串聯電容器 C (簡易的)：**a. 充電**($q_0 = 0$) $q = C\varepsilon(1 - e^{-t/\tau})$ ；**b. 放電**($q_0 = C\varepsilon$) $q = C\varepsilon e^{-t/\tau}$ ；**c. 時間常數** $\tau \equiv RC$ ；**d. 電容器充電時**，電阻器及電容器各分享一半電源提供之能量。

Note 電容器如未帶電(如剛充電時)， $V_C = 0$ ，即**短路**，等效電阻 $R_C = 0$ ；若飽和充電， $I_C = 0$ ，即**斷路**，等效電阻 $R_C \rightarrow \infty$ 。電容器充電或放電時其帶電量及電壓與時間關係為指數的。

伏特計(等效電阻 $R_V \rightarrow \infty$)測電壓用，聯接須**並聯**；**安培計**(等效電阻 $R_A \rightarrow 0$)測電流用，聯接須**串聯**。

須採取何種預防措施才能防止此類火災？

direct-current (DC) circuits 直流電路; device 裝置, 器件; electromotive force (emf) 電動勢; rechargeable 可充電的; loop 迴路(線); junction/node 節點; ground 接地; hot/neutral line 火/中性線; voltage 電壓, 伏特數; (capacitive) time constant (電容)時間常數; ammeter 安培計; voltmeter 伏特計; polarized plug 極性插頭; electrical engineering 電機工程; electric grid 電力網; electric generator 發電機; pit stop 修理站; electric eel 電鰻; Q&A. 電鰻如何發電? 為什麼不會電到自己? 科學人 2006 年 4 月號。*鋰電池：安全不起火，科學人 2007 年 1 月。●備忘錄●